

CS 61C: Great Ideas in Computer  
Architecture (Machine Structures)  
Single-Cycle CPU  
*Datapath Control Part 1*

Instructors:

Krste Asanovic & Vladimir Stojanovic

<http://inst.eecs.berkeley.edu/~cs61c/>

# Review

- Timing constraints for Finite State Machines
  - Setup time, Hold Time, Clock to Q time
- Use muxes to select among inputs
  - S control bits selects from  $2^S$  inputs
  - Each input can be n-bits wide, indep of S
  - Can implement muxes hierarchically
- ALU can be implemented using a mux
  - Coupled with basic block elements

# How to design Adder/Subtractor?

- Truth-table, then determine canonical form, then minimize and implement as we've seen before
- Look at breaking the problem down into smaller pieces that we can cascade or hierarchically layer

# Adder/Subtractor – One-bit adder LSB...

	$a_3$	$a_2$	$a_1$	$a_0$
+	$b_3$	$b_2$	$b_1$	$b_0$
<hr/>				
	$s_3$	$s_2$	$s_1$	$s_0$

$a_0$	$b_0$	$s_0$	$c_1$
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$s_0 =$$

$$c_1 =$$

# Adder/Subtractor – One-bit adder

(1/2)...



$a_i$	$b_i$	$c_i$	$s_i$	$c_{i+1}$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

	$a_3$	$a_2$	$a_1$	$a_0$
+	$b_3$	$b_2$	$b_1$	$b_0$
	$s_3$	$s_2$	$s_1$	$s_0$

$$s_i =$$


$$c_{i+1} =$$

# Adder/Subtractor – One-bit adder (2/2)

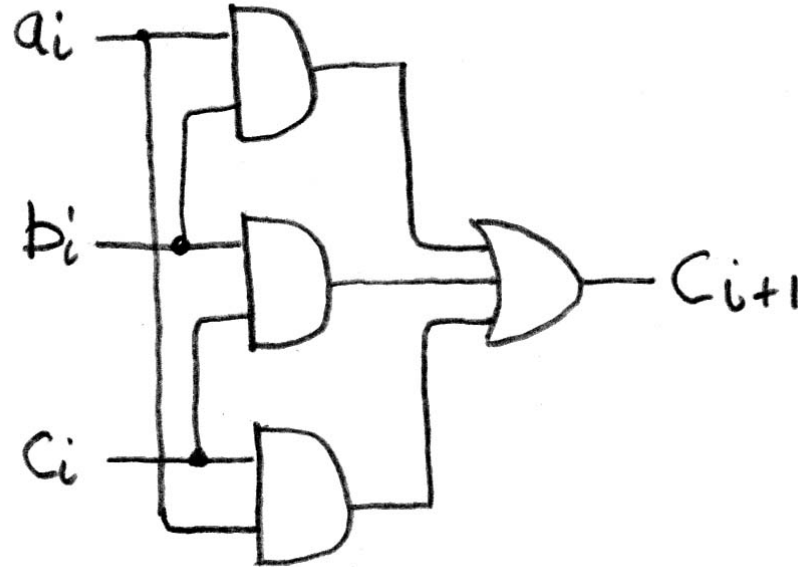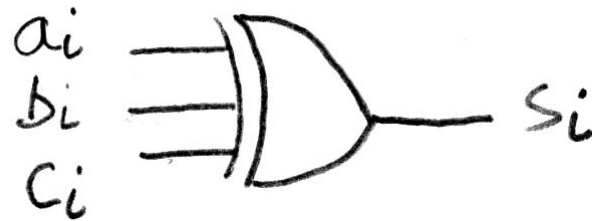

$$s_i = \text{XOR}(a_i, b_i, c_i)$$
$$c_{i+1} = \text{MAJ}(a_i, b_i, c_i) = a_i b_i + a_i c_i + b_i c_i$$

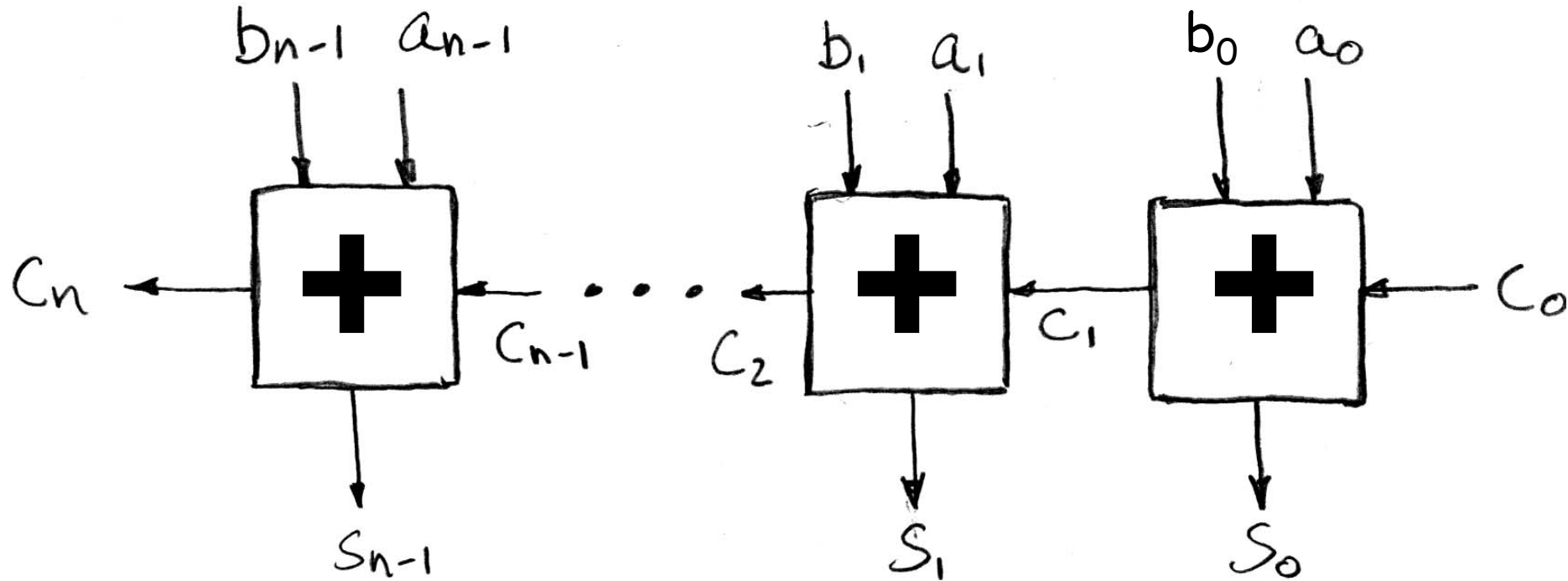
N 1-bit adders  $\Rightarrow$  1 N-bit adder



**What about overflow?**

**Overflow =  $c_n$ ?**

# Extremely Clever Subtractor

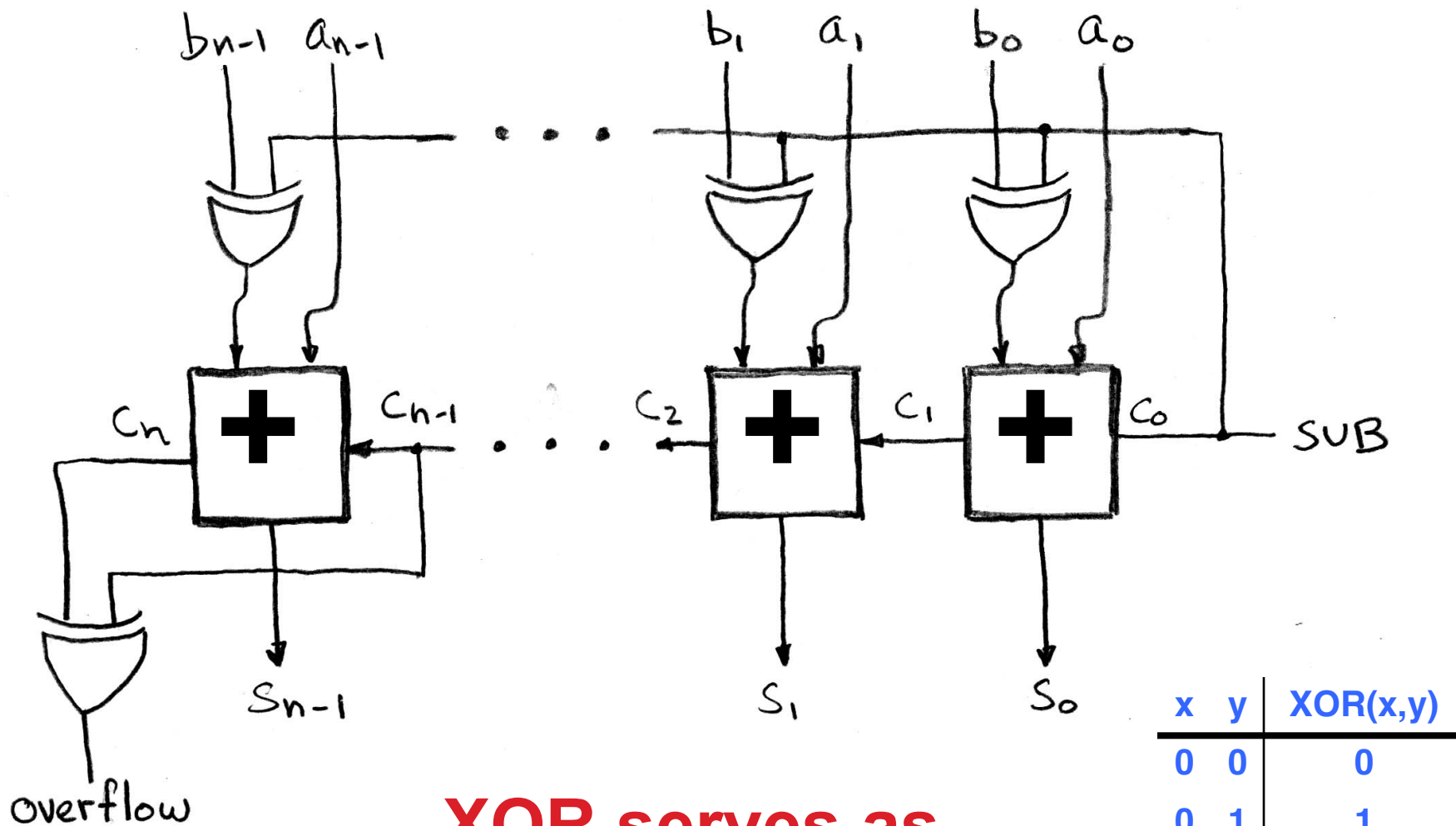


**XOR serves as  
conditional inverter!**

x	y	XOR(x,y)
0	0	0
0	1	1
1	0	1
1	1	0



# Components of a Computer

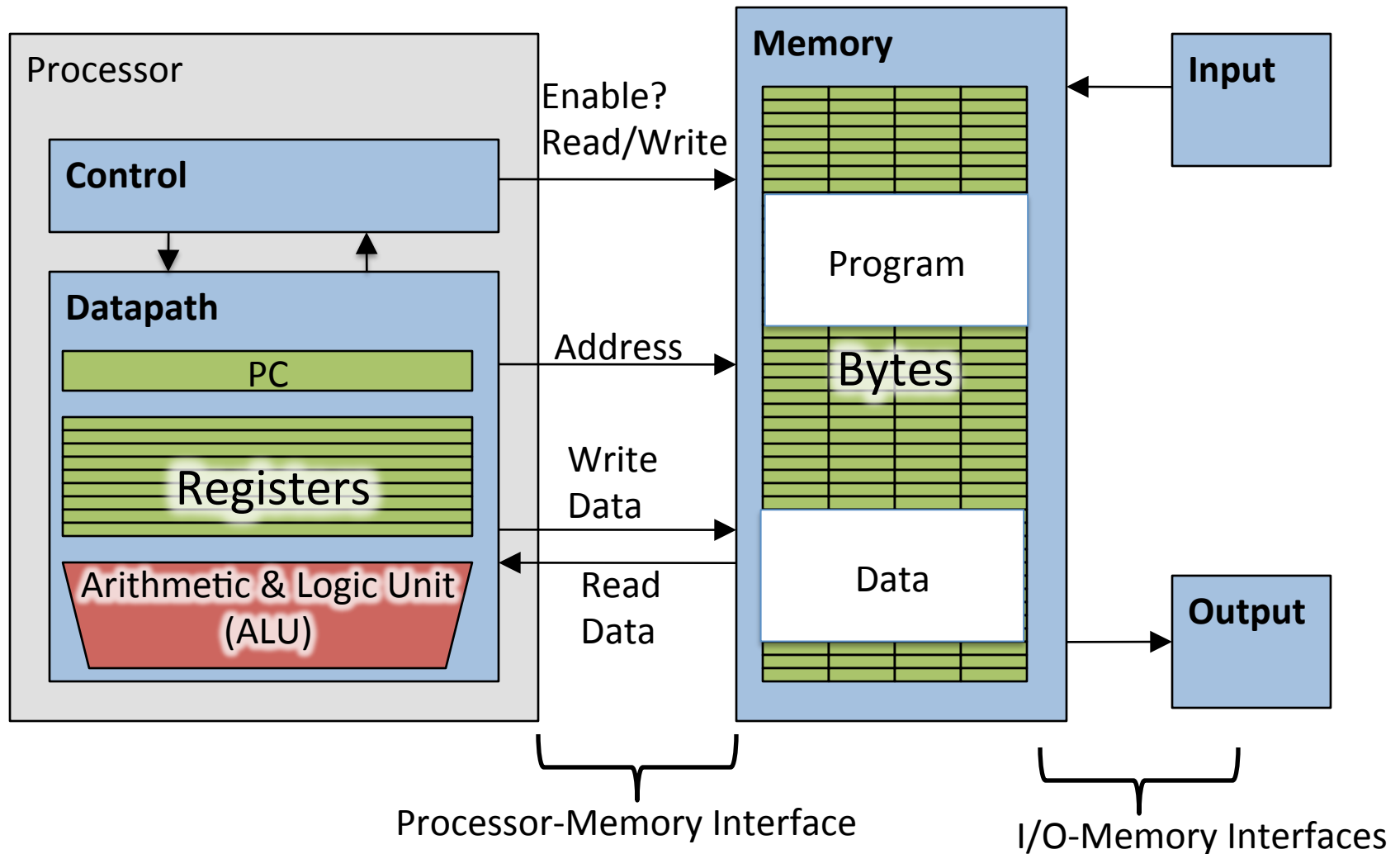

# The CPU

- Processor (CPU): the active part of the computer that does all the work (data manipulation and decision-making)
- Datapath: portion of the processor that contains hardware necessary to perform operations required by the processor (the brawn)
- Control: portion of the processor (also in hardware) that tells the datapath what needs to be done (the brain)

# Five Stages of Instruction Execution

- Stage 1: Instruction Fetch
- Stage 2: Instruction Decode
- Stage 3: ALU (Arithmetic-Logic Unit)
- Stage 4: Memory Access
- Stage 5: Register Write

# Stages of Execution (1/5)

- There is a wide variety of MIPS instructions: so what general steps do they have in common?
- Stage 1: Instruction Fetch
  - no matter what the instruction, the 32-bit instruction word must first be fetched from memory (the cache-memory hierarchy)
  - also, this is where we Increment PC (that is,  $PC = PC + 4$ , to point to the next instruction: byte addressing so + 4)

# Stages of Execution (2/5)

- Stage 2: Instruction Decode
  - upon fetching the instruction, we next gather data from the fields (decode all necessary instruction data)
  - first, read the opcode to determine instruction type and field lengths
  - second, read in data from all necessary registers
    - for add, read two registers
    - for addi, read one register
    - for jal, no reads necessary

# Stages of Execution (3/5)

- Stage 3: ALU (Arithmetic-Logic Unit)
  - the real work of most instructions is done here: arithmetic (+, -, \*, /), shifting, logic (&, |), comparisons (slt)
  - what about loads and stores?
    - lw \$t0, 40(\$t1)
    - the address we are accessing in memory = the value in \$t1 PLUS the value 40
    - so we do this addition in this stage

# Stages of Execution (4/5)

- Stage 4: Memory Access
  - actually only the load and store instructions do anything during this stage; the others remain idle during this stage or skip it all together
  - since these instructions have a unique step, we need this extra stage to account for them
  - as a result of the cache system, this stage is expected to be fast


# Stages of Execution (5/5)

- Stage 5: Register Write
  - most instructions write the result of some computation into a register
  - examples: arithmetic, logical, shifts, loads, slt
  - what about stores, branches, jumps?
    - don't write anything into a register at the end
    - these remain idle during this fifth stage or skip it all together



# Administrivia


# Stages of Execution on Datapath

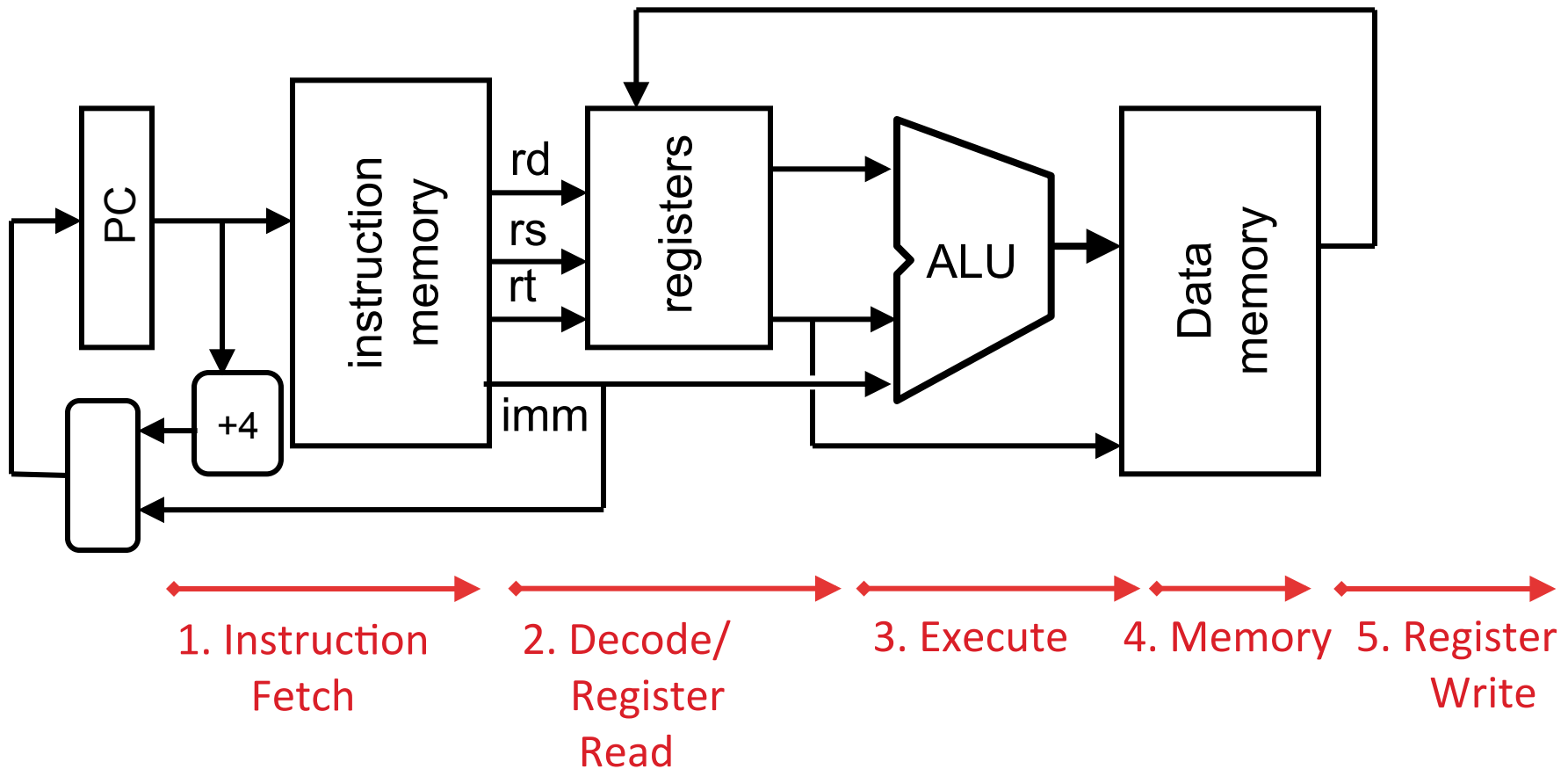

# Datapath Walkthroughs (1/3)

- add \$r3,\$r1,\$r2 #  $r3 = r1 + r2$ 
  - Stage 1: fetch this instruction, increment PC
  - Stage 2: decode to determine it is an add, then read registers \$r1 and \$r2
  - Stage 3: add the two values retrieved in Stage 2
  - Stage 4: idle (nothing to write to memory)
  - Stage 5: write result of Stage 3 into register \$r3


# Example: add Instruction

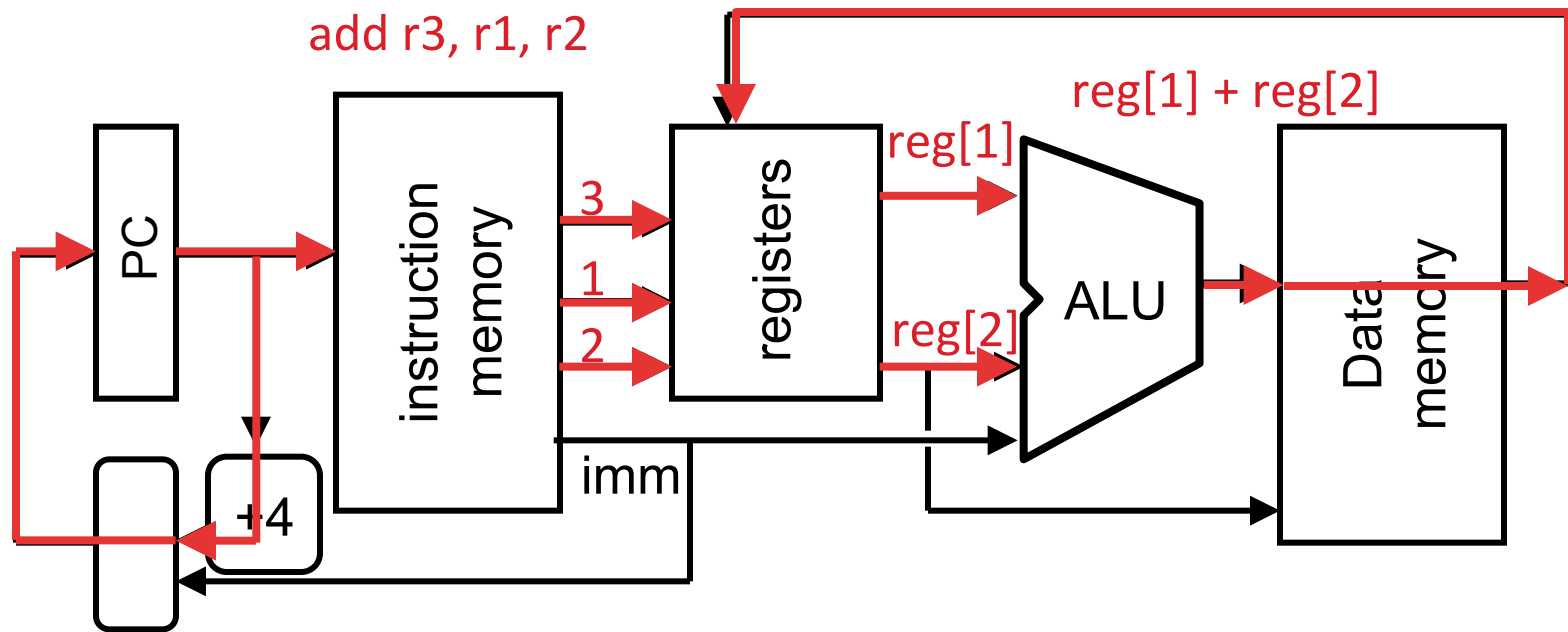

# Datapath Walkthroughs (2/3)

- `slti $r3,$r1,17`  
# if ( $r1 < 17$ )  $r3 = 1$  else  $r3 = 0$ 
  - Stage 1: fetch this instruction, increment PC
  - Stage 2: decode to determine it is an `slti`, then read register `$r1`
  - Stage 3: compare value retrieved in Stage 2 with the integer 17
  - Stage 4: idle
  - Stage 5: write the result of Stage 3 (1 if reg source was less than signed immediate, 0 otherwise) into register `$r3`


# Example: slti Instruction

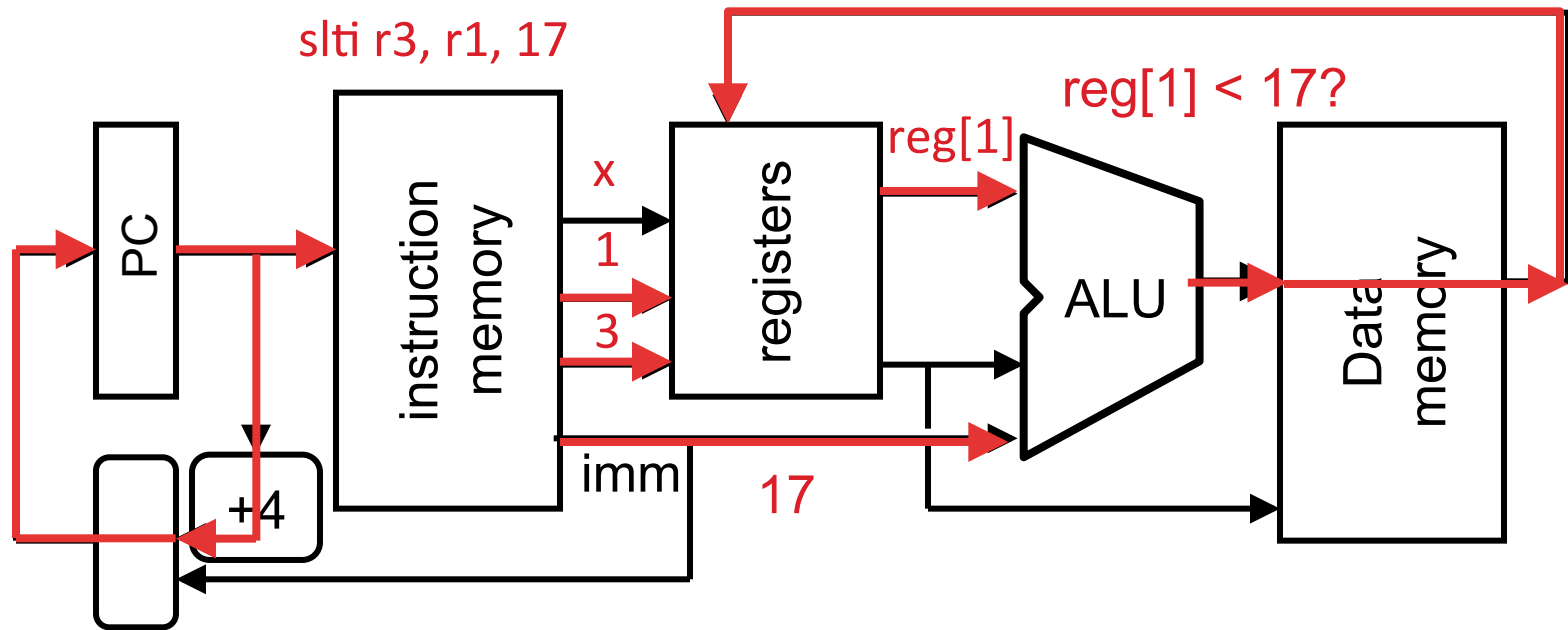

# Datapath Walkthroughs (3/3)

- `sw $r3,17($r1) # Mem[r1+17]=r3`
  - Stage 1: fetch this instruction, increment PC
  - Stage 2: decode to determine it is a sw, then read registers \$r1 and \$r3
  - Stage 3: add 17 to value in register \$r1 (retrieved in Stage 2) to compute address
  - Stage 4: write value in register \$r3 (retrieved in Stage 2) into memory address computed in Stage 3
  - Stage 5: idle (nothing to write into a register)

# Example: sw Instruction

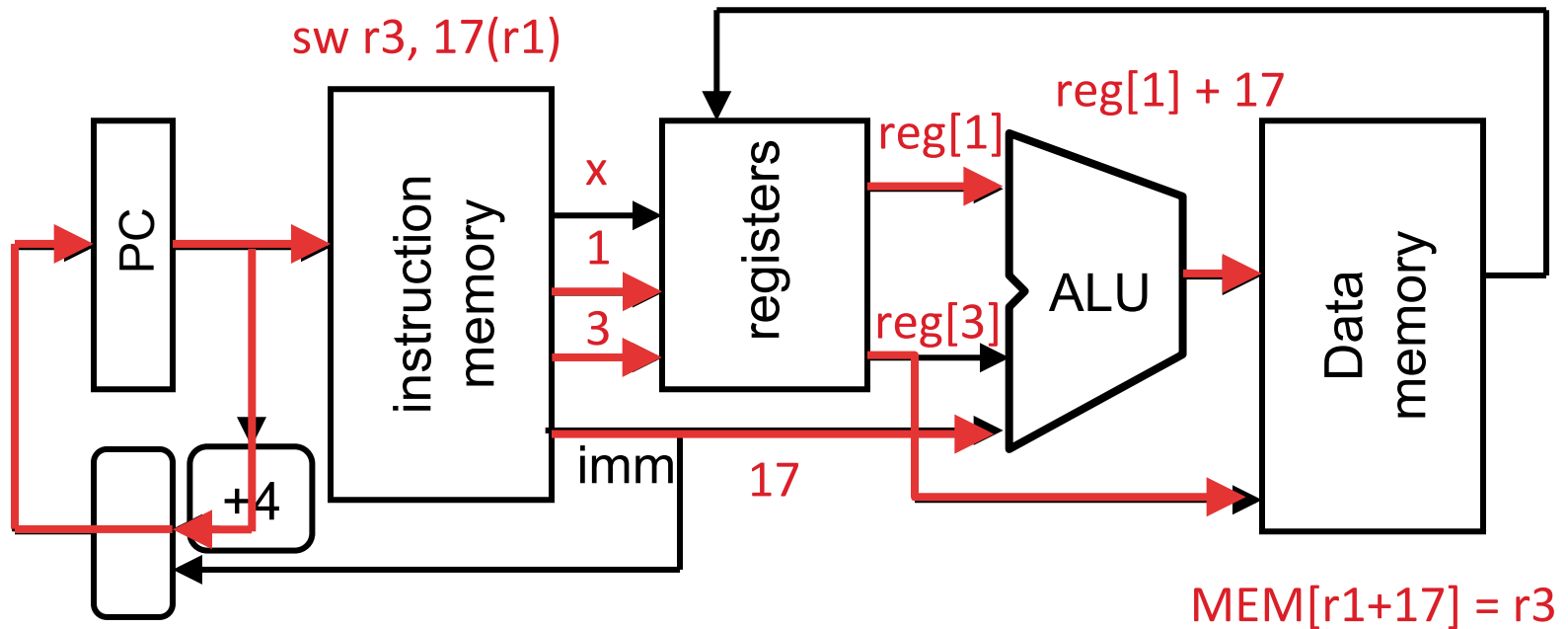




# Why Five Stages? (1/2)

- Could we have a different number of stages?
  - Yes, other ISAs have different natural number of stages
- Why does MIPS have five if instructions tend to idle for at least one stage?
  - Five stages are the union of all the operations needed by all the instructions.
  - One instruction uses all five stages: the load

## Why Five Stages? (2/2)


- `lw $r3,17($r1) # r3=Mem[r1+17]`
  - Stage 1: fetch this instruction, increment PC
  - Stage 2: decode to determine it is a `lw`, then read register `$r1`
  - Stage 3: add 17 to value in register `$r1` (retrieved in Stage 2)
  - Stage 4: read value from memory address computed in Stage 3
  - Stage 5: write value read in Stage 4 into register `$r3`

# Example: lw Instruction

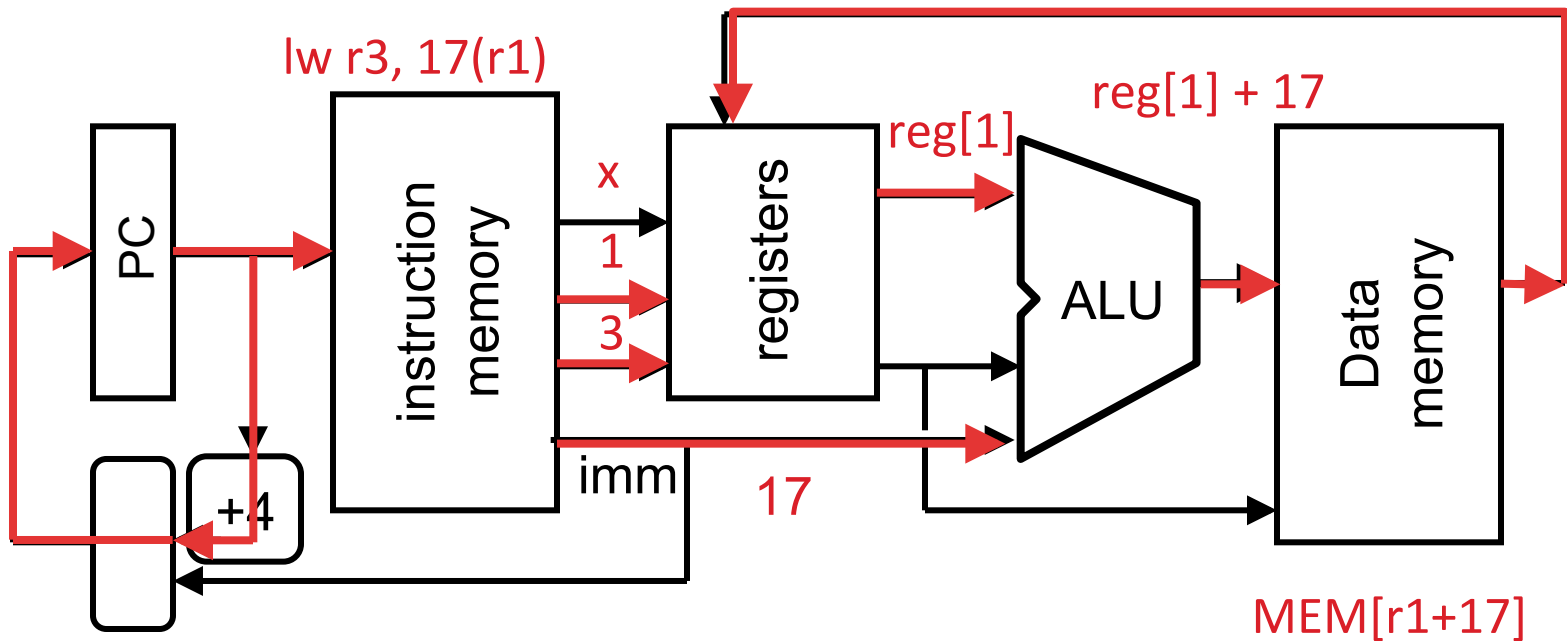
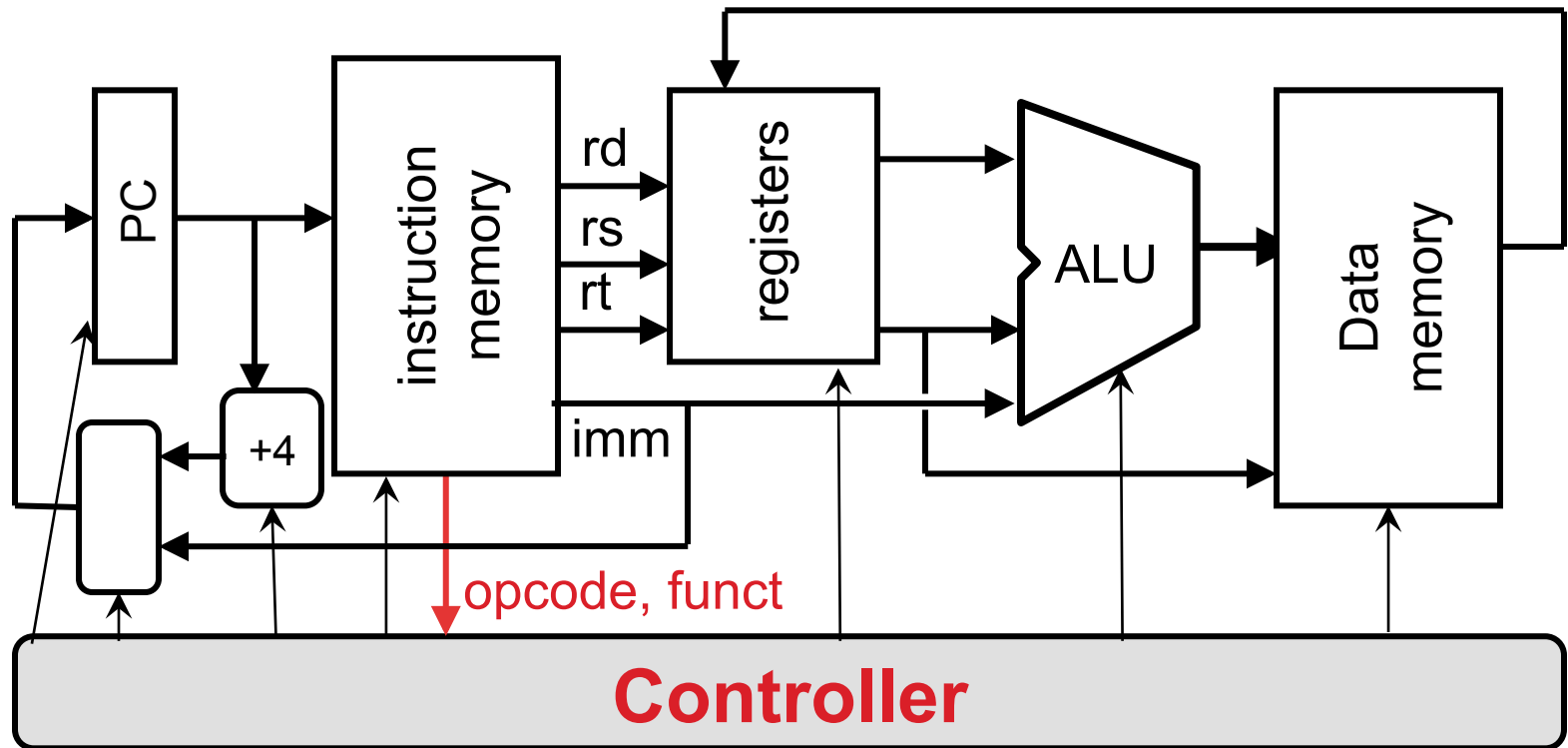
# Datapath and Control

- Datapath designed to support data transfers required by instructions
- Controller causes correct transfers to happen



# In the News

- At ISSCC 2015 in San Francisco yesterday, latest IBM mainframe chip details
- z13 designed in 22nm SOI technology with **seventeen** metal layers, 4 billion transistors/chip
- 8 cores/chip, with 2MB L2 cache, 64MB L3 cache, and 480MB L4 cache.
- 5GHz clock rate, 6 instructions per cycle, 2 threads/core
- Up to 24 processor chips in shared memory node



SanDisk®



Seagate



Register Now:

Berkeley –  
IAP  
Workshop on  
the  
Future of  
Cloud  
Technologies

Friday,  
February 27,  
2015



- ❑ POSTERS: \$500 Prizes for Best Undergrad & Best Grad
- ❑ CAREER FAIR: During Lunch/Breaks, Bring Your Resume  
<http://www.industry-academia.org/event-berkeley-cloud-workshop.html>



### Quotes from the MIT Workshop

**"I was excited by the turnout and the breadth of the speakers."** – Prof. Matei Zaharia, CTO Databricks

**"In a nutshell, the workshop is an excellent opportunity for students, faculties and people from industry to share ideas."** – Po-An Tsai, PhD Student, MIT CSAIL, Best Poster Award

# Processor Design: 5 steps

Step 1: Analyze instruction set to determine datapath requirements

- Meaning of each instruction is given by register transfers
- Datapath must include storage element for ISA registers
- Datapath must support each register transfer

Step 2: Select set of datapath components & establish clock methodology


Step 3: Assemble datapath components that meet the requirements

Step 4: Analyze implementation of each instruction to determine setting of control points that realizes the register transfer

Step 5: Assemble the control logic
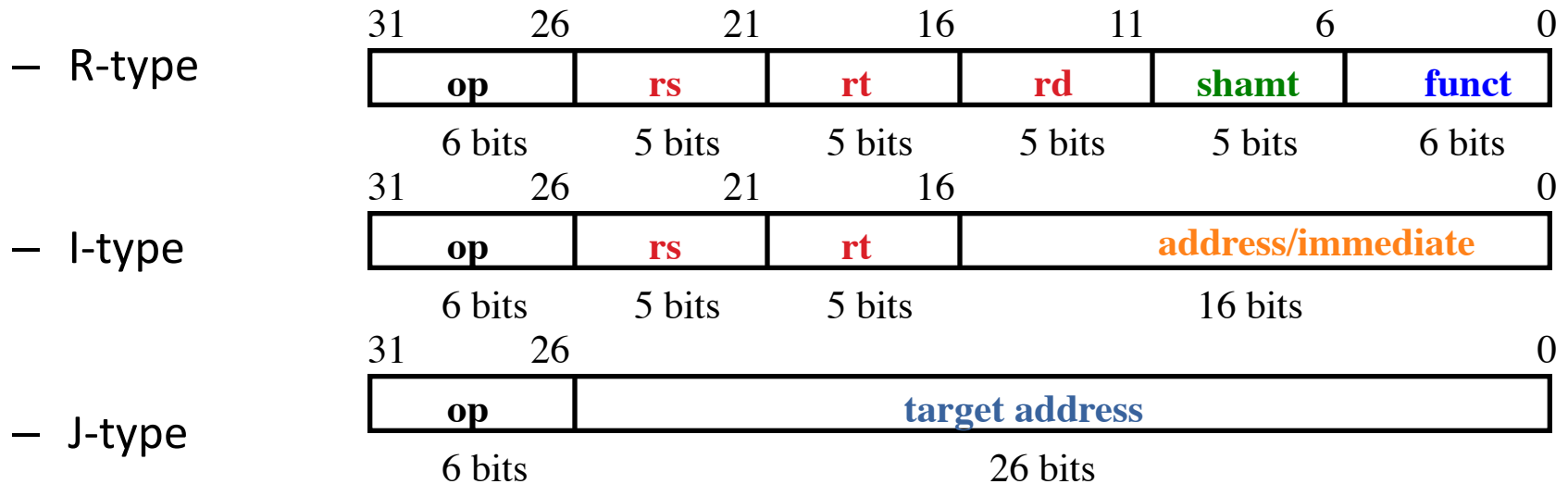
# The MIPS Instruction Formats

- All MIPS instructions are 32 bits long. 3 formats:



- The different fields are:
  - **op**: operation (“opcode”) of the instruction
  - **rs, rt, rd**: the source and destination register specifiers
  - **shamt**: shift amount
  - **funct**: selects the variant of the operation in the “op” field
  - **address / immediate**: address offset or immediate value
  - **target address**: target address of jump instruction




# The MIPS-lite Subset

- ADDU and SUBU


- `addu rd,rs,rt`

- `subu rd,rs,rt`

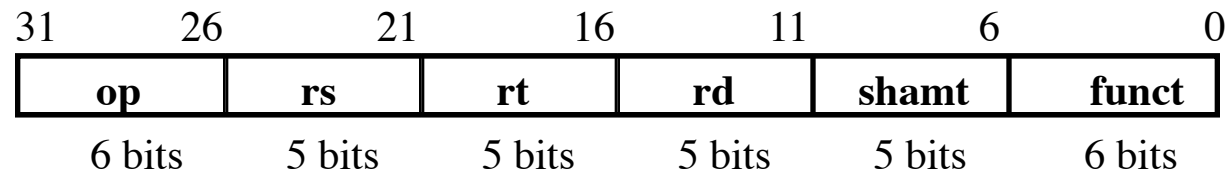

- OR Immediate:

- `ori rt,rs,imm16`

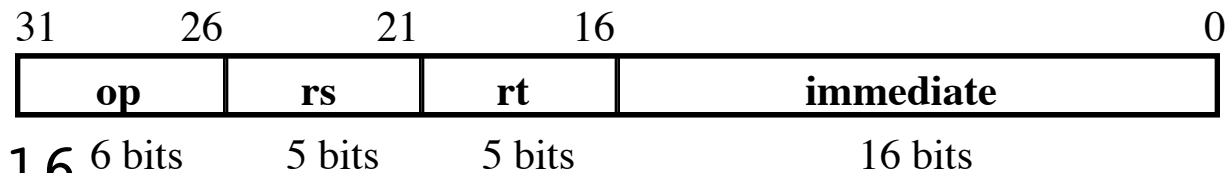


- LOAD and

STORE Word


- `lw rt,rs,imm16`

- `sw rt,rs,imm16`

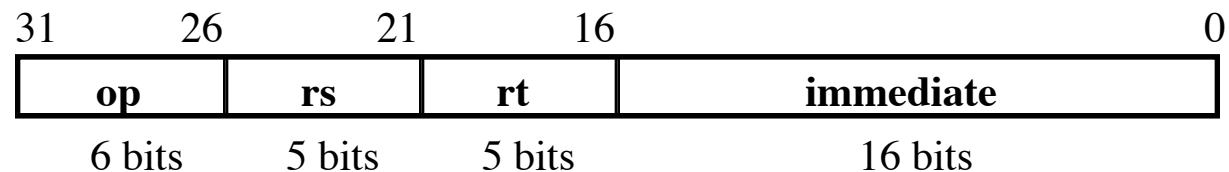

- BRANCH:

- `beq rs,rt,imm16`

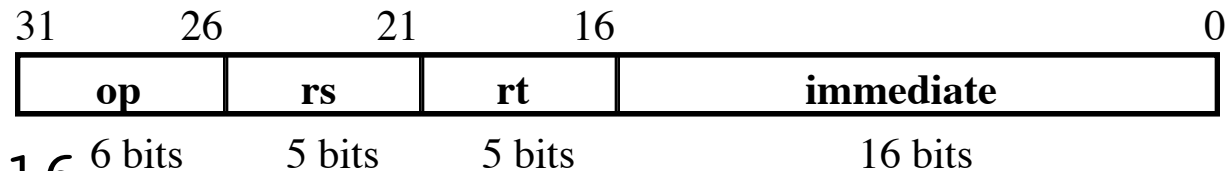

# Register Transfer Level (RTL)

- Colloquially called “Register Transfer Language”
- RTL gives the meaning of the instructions
- All start by fetching the instruction itself

```
{op , rs , rt , rd , shamt , funct} ← MEM[ PC ]
```

```
{op , rs , rt , Imm16} ← MEM[ PC ]
```

## Inst    Register Transfers

```
ADDU    R[rd] ← R[rs] + R[rt]; PC ← PC + 4
```

```
SUBU    R[rd] ← R[rs] - R[rt]; PC ← PC + 4
```

```
ORI     R[rt] ← R[rs] | zero_ext(Imm16); PC ← PC + 4
```

```
LOAD    R[rt] ← MEM[ R[rs] + sign_ext(Imm16) ]; PC ← PC + 4
```

```
STORE   MEM[ R[rs] + sign_ext(Imm16) ] ← R[rt]; PC ← PC + 4
```




```
BEQ     if ( R[rs] == R[rt] )  
         PC ← PC + 4 + {sign_ext(Imm16), 2'b00}  
      else PC ← PC + 4
```

# Step 1: Requirements of the Instruction Set

- Memory (MEM)
  - Instructions & data (will use one for each)
- Registers (R: 32, 32-bit wide registers)
  - Read RS
  - Read RT
  - Write RT or RD
- Program Counter (PC)
- Extender (sign/zero extend)
- Add/Sub/OR/etc unit for operation on register(s) or extended immediate (ALU)
- Add 4 (+ maybe extended immediate) to PC
- Compare registers?
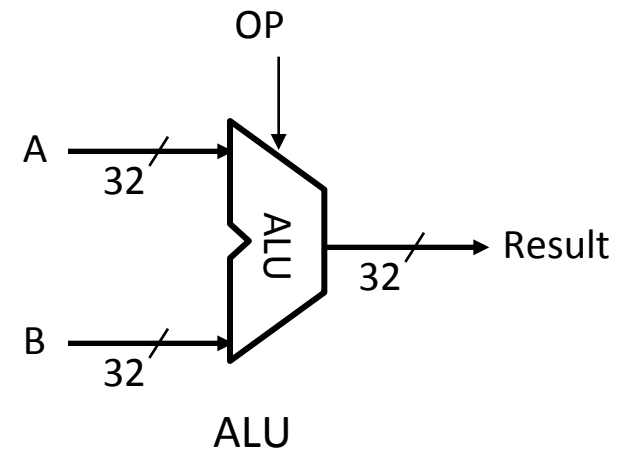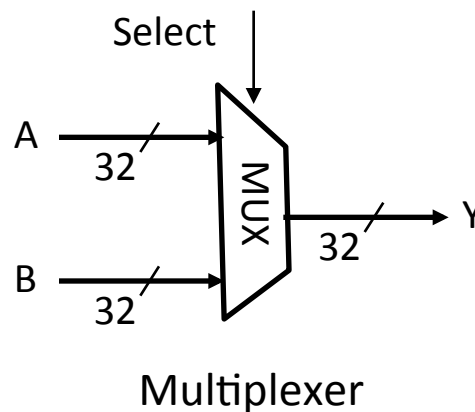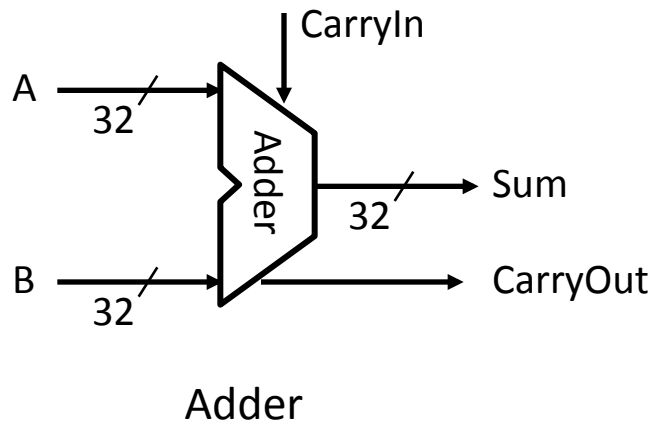
# Step 2: Components of the Datapath

- Combinational Elements
- Storage Elements + Clocking Methodology
- Building Blocks



# ALU Needs for MIPS-lite + Rest of MIPS

- Addition, subtraction, logical OR, ==:

ADDU  $R[rd] = R[rs] + R[rt]; \dots$

SUBU  $R[rd] = R[rs] - R[rt]; \dots$


ORI  $R[rt] = R[rs] \mid \text{zero\_ext}(\text{Imm16}) \dots$

BEQ  $\text{if } (R[rs] == R[rt]) \dots$

- Test to see if output == 0 for any ALU operation gives == test. How?
- P&H also adds AND, Set Less Than (1 if  $A < B$ , 0 otherwise)
- ALU follows Chapter 5

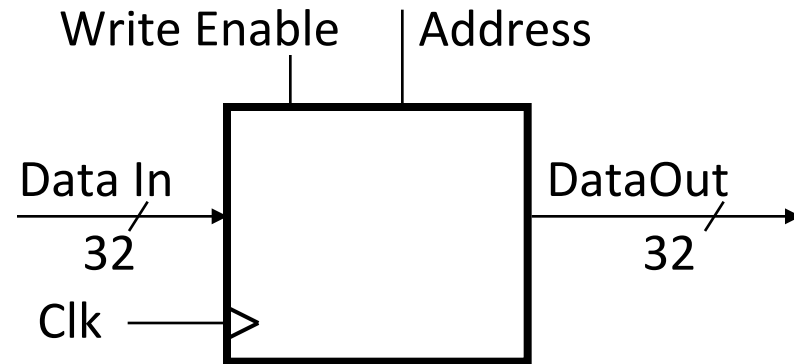
# Storage Element: Idealized Memory

- “Magic” Memory
  - One input bus: Data In
  - One output bus: Data Out
- Memory word is found by:
  - For Read: Address selects the word to put on Data Out
  - For Write: Set Write Enable = 1: address selects the memory word to be written via the Data In bus
- Clock input (CLK)
  - CLK input is a factor ONLY during write operation
  - During read operation, behaves as a combinational logic block: Address valid  $\Rightarrow$  Data Out valid after “access time”



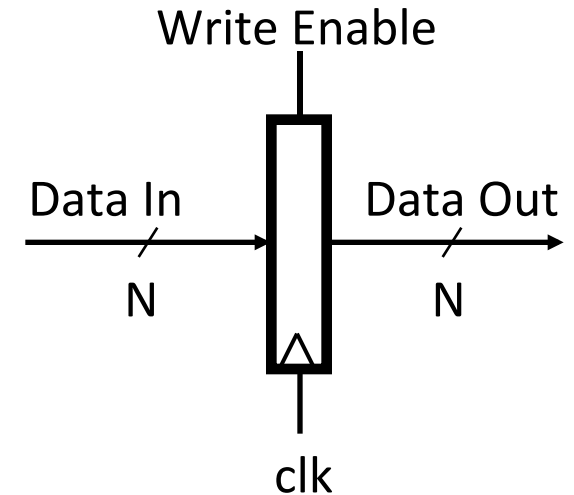
# Storage Element: Register (Building Block)

- Similar to D Flip Flop except
  - N-bit input and output
  - Write Enable input
- Write Enable:
  - Negated (or deasserted) (0): Data Out will not change
  - Asserted (1): Data Out will become Data In on positive edge of clock


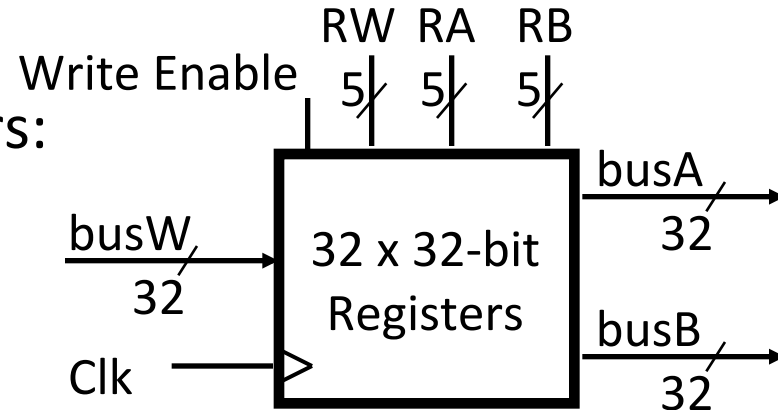
# Storage Element: Register File


- Register File consists of 32 registers:
  - Two 32-bit output busses: busA and busB
  - One 32-bit input bus: busW
- Register is selected by:
  - RA (number) selects the register to put on busA (data)
  - RB (number) selects the register to put on busB (data)
  - RW (number) selects the register to be written via busW (data) when Write Enable is 1
- Clock input (clk)
  - Clk input is a factor ONLY during write operation
  - During read operation, behaves as a combinational logic block:
    - RA or RB valid  $\Rightarrow$  busA or busB valid after “access time.”





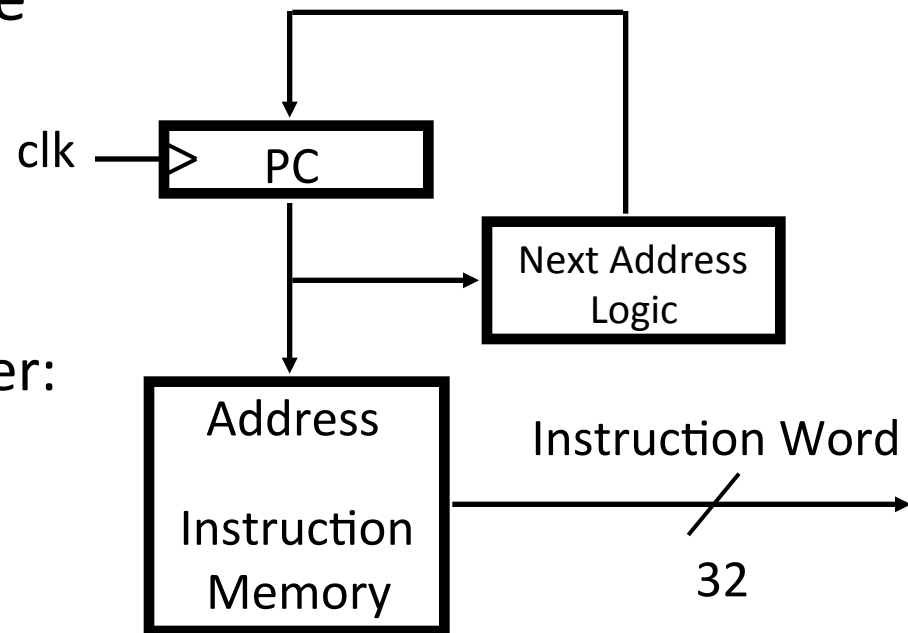
# Step 3a: Instruction Fetch Unit

- Register Transfer Requirements  $\Rightarrow$  Datapath Assembly
- Instruction Fetch
- Read Operands and Execute Operation
- Common RTL operations
  - Fetch the Instruction:  
 $\text{mem}[\text{PC}]$
  - Update the program counter:
    - Sequential Code:  
 $\text{PC} \leftarrow \text{PC} + 4$
    - Branch and Jump:  
 $\text{PC} \leftarrow \text{“something else”}$



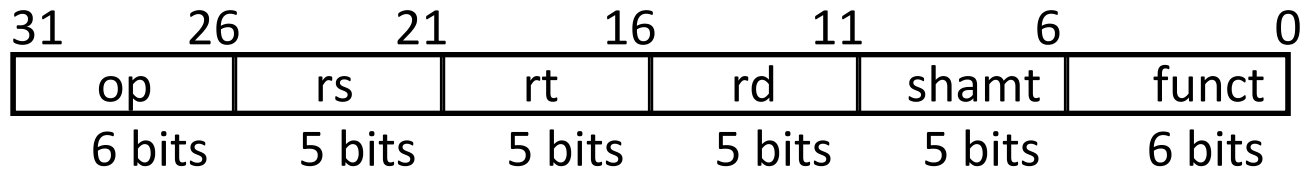
# Step 3b: Add & Subtract

- $R[rd] = R[rs] \text{ op } R[rt]$  (`addu rd,rs,rt`)
  - Ra, Rb, and Rw come from instruction's Rs, Rt, and Rd fields




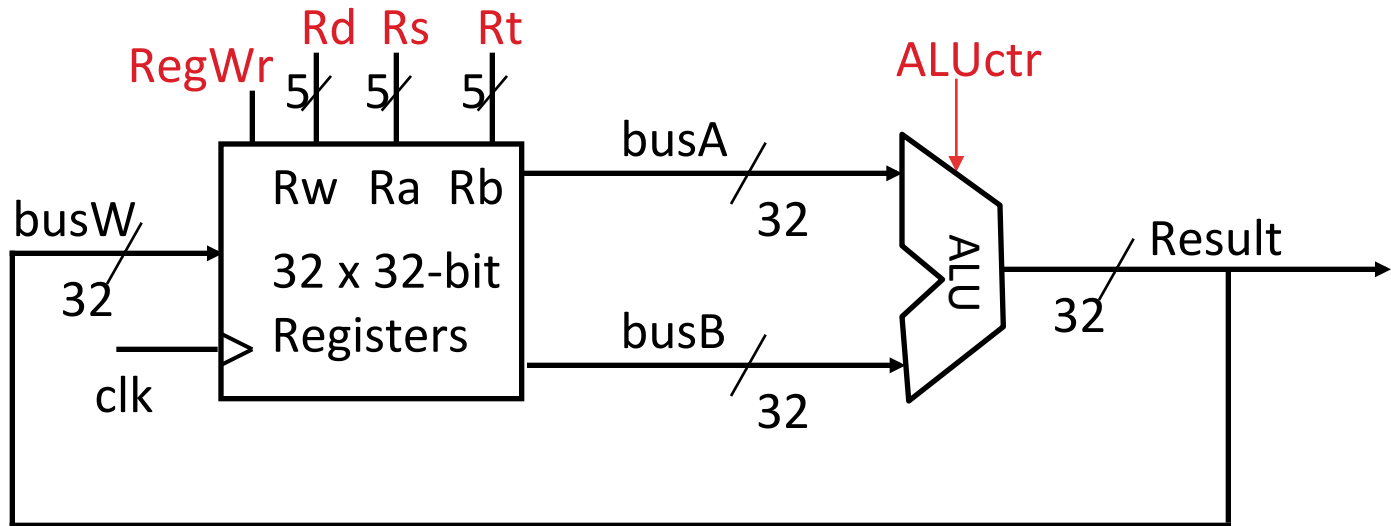- **ALUctr** and **RegWr**: control logic after decoding the instruction




- ... Already defined the register file & ALU

# Clocking Methodology

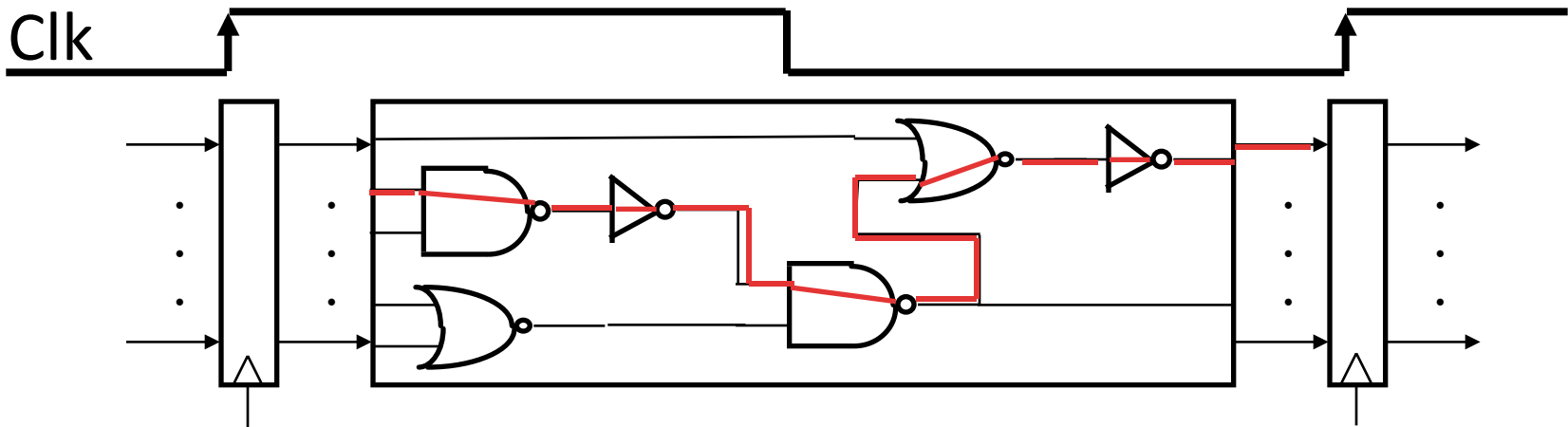


- Storage elements clocked by same edge
- Flip-flops (FFs) and combinational logic have some delays
  - Gates: delay from input change to output change
  - Signals at FF D input must be stable before active clock edge to allow signal to travel within the FF (set-up time), and we have the usual clock-to-Q delay
- “Critical path” (longest path through logic) determines length of clock period
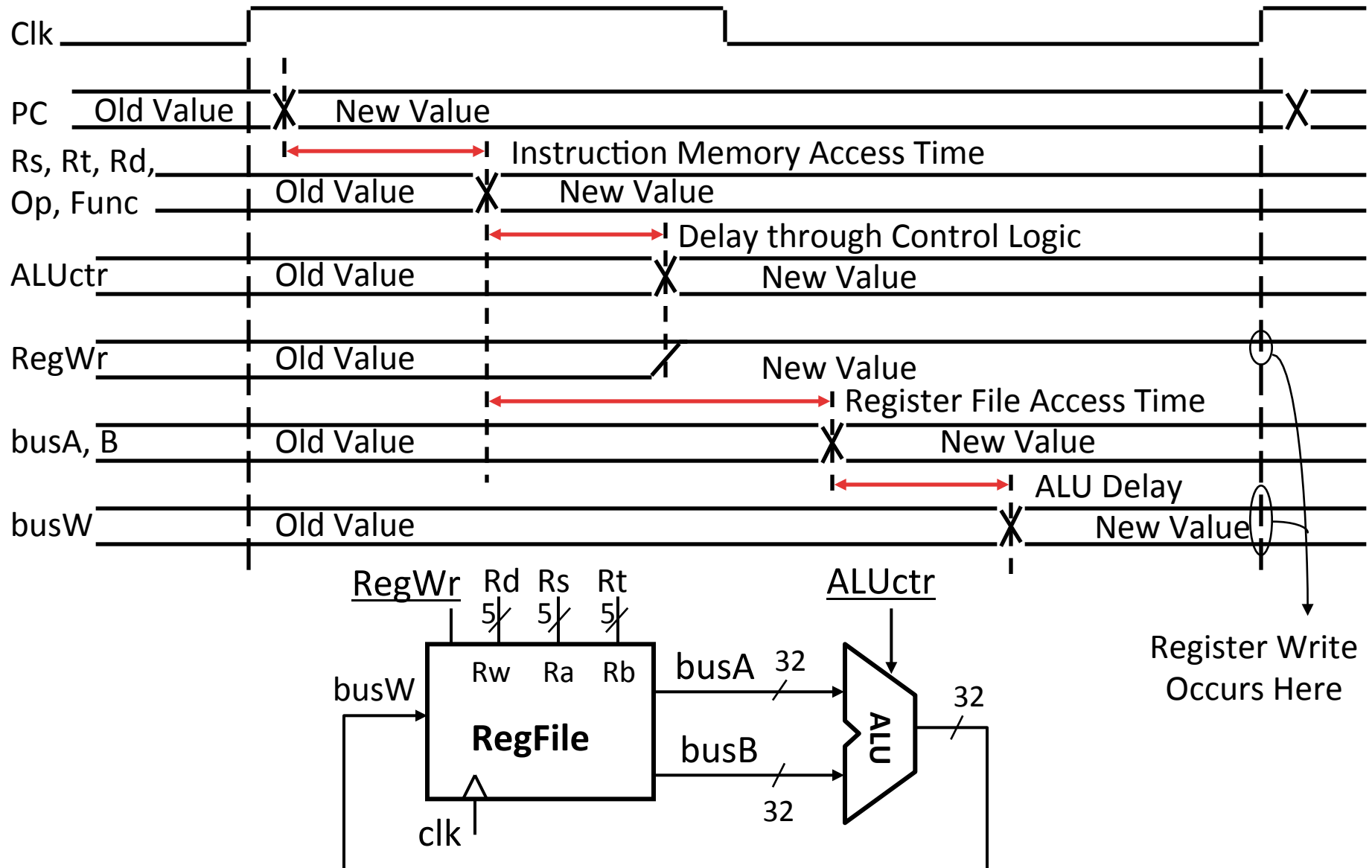
# Register-Register Timing: One Complete Cycle


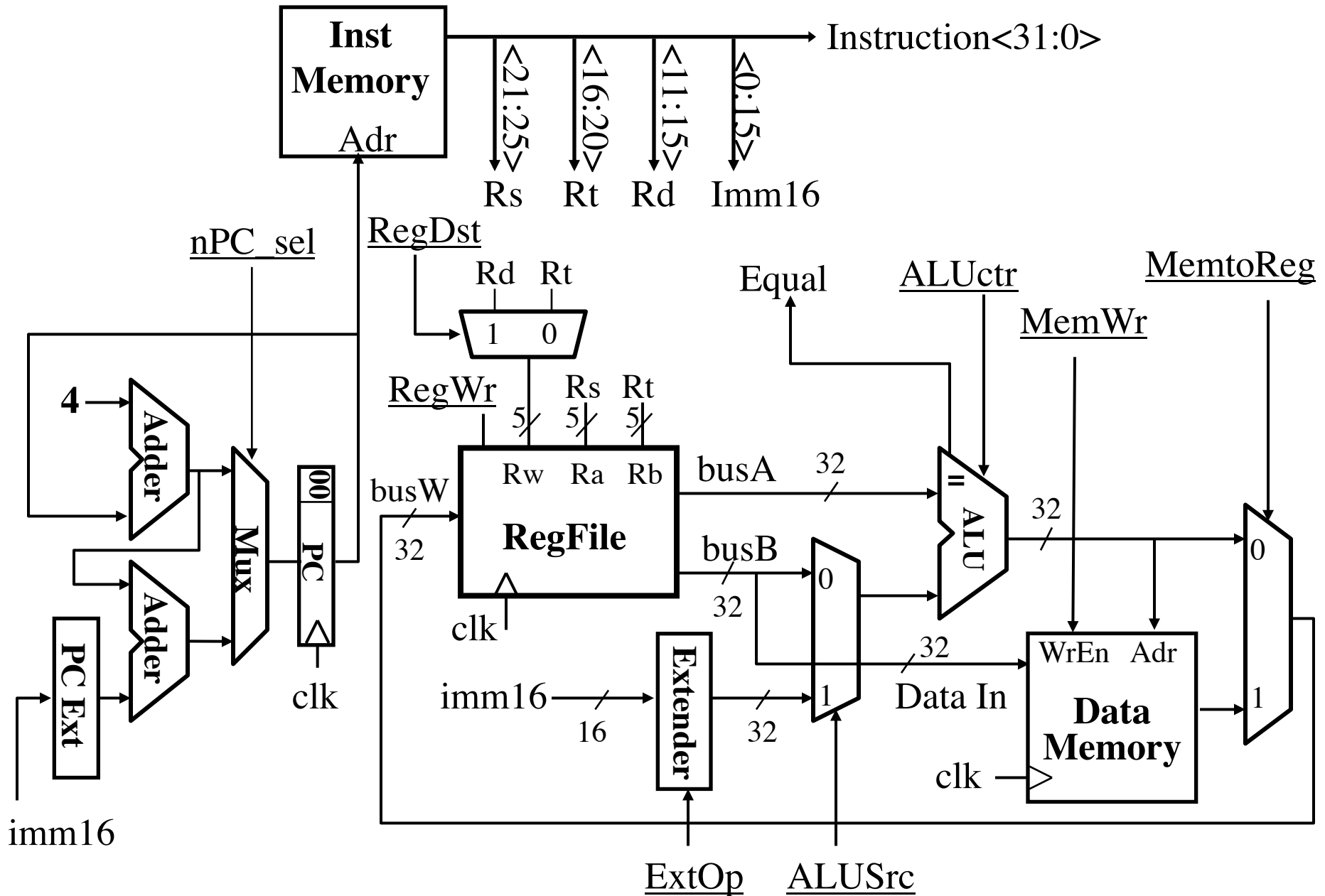
# Putting it All Together: A Single Cycle Datapath



# Peer Instruction

- A. Our ALU is a synchronous device
- B. We should use the main ALU to compute  $PC = PC + 4$
- C. The ALU is inactive for memory reads or writes.

Option	1	2	3
A	F	F	F
A	T	T	T
B	F	T	F
C	F	T	T
C	T	F	F
D	T	F	T
E	T	T	F
E	F	F	T

# Processor Design: 3 of 5 steps

Step 1: Analyze instruction set to determine datapath requirements

- Meaning of each instruction is given by register transfers
- Datapath must include storage element for ISA registers
- Datapath must support each register transfer

Step 2: Select set of datapath components & establish clock methodology

Step 3: Assemble datapath components that meet the requirements

Step 4: Analyze implementation of each instruction to determine setting of control points that realizes the register transfer

Step 5: Assemble the control logic

# In Conclusion

- “Divide and Conquer” to build complex logic blocks from smaller simpler pieces (adder)
- Five stages of MIPS instruction execution
- Mapping instructions to datapath components
- Single long clock cycle per instruction